

LabMate — Lab Record

Student: Test Student
Roll No: 20P31A1234
Experiment: Zener Diode Characteristics
Lab: Physics Lab
Completed On: 12/5/2026

AIM

To study the V-I characteristics of a Zener diode.

PROCEDURE

1. Connect circuit
2. Turn on power
3. Record readings

OBSERVATION TABLE

Forward Bias Readings

SUPPLYV	VZ	I
0.1	0.1	0.001
0.5	0.5	0.01
1	0.7	5

Reverse Bias Readings

SUPPLYV	VZ	I
2	-2	-0.001
5	-5	-0.01
6	-5.1	-2

RESULT

Everything worked as expected.